

Achhruram Memorial College

Affiliated to Sidho Kanho Birsha University

Electronics Examination

Question – 3

Date: 13-11-2017

Time: 10:30AM – 12.30PM

Full Marks: 50

All Questions are compulsory:

- (1) How can drain current in a MOSFET be enhanced by a negative gate voltage? 2
- (2) Draw the logic circuit diagram of Boolean expression $(\bar{A} + B)A\bar{B} = Y$ 2
- (3) How do the characterizations of a practical OP-AMP differ from those of ideal OP-AMP? 2
- (4) Show that an amplifier having an input (v_i)-Output (V_o), the characteristic given as, $v_o = a_1v_i + a_2v_i^2$, where a_1 and a_2 are constants, can be used to design an amplitude modulator. 2
- (4) What is Karnaugh Map representation? Find the Karnaugh Map representation of following equation : $Y = ABCD + \bar{A}BCD + A\bar{B}CD + \bar{A}\bar{B}CD$ 2
- (5) What is the Barkhausen criterion for a feedback amplifier to function as an oscillator? With the help of a circuit diagram, explain the operation of a phase shift oscillator and find its frequency of oscillation. 1+4
- (6) What is a tunnel diode? Explain the I-V characteristics of tunnel diode. What is the significance of the negative resistance shown by the diode? 1+2+2
- (7) What is an R-S flip-flop? Give its logic symbol, truth table, and circuit realization using NOR/NAND gates. How R-S flip-flop can be converted to J-K flip-flop? 1+3+1
- (7) What is an MOSFET? What is the main difference between MOSFET and JFET? Determine the output voltage of the JFET amplifier with $v_i = 1\text{mV}$ and $R_D = 2.5\text{k}\Omega$. Take $g_m = 5\text{mA/V}$ and $r_d = 60\text{k}\Omega$ (Symbols have usual meaning) 1+2+2
- (8) (a) Obtain an expression for the output voltage of a differential amplifier in terms of A_d and A_c (where A_d : differential voltage gain and A_c : Common mode voltage gain).
- (b) What is amplitude modulation? Deduce an expression for an amplitude modulated carrier wave. Show that amplitude modulated wave can be represented by a carrier wave and two side band frequencies. Deduce the expression of powers of these three components.
- (c) A 5kW carrier wave is amplitude modulated to a modulated index 60%. Find the total power in the amplitude modulated wave. $(2+1)+(1+2+2)+2$
- (10) (a) Draw a circuit diagram of two stage RC-coupled CE transistor amplifier. Show how the magnitude and the phase angle of its voltage gain vary with frequency. Qualitatively explain these variations. Define the half power frequencies.
- (b) If the lower and upper half-power frequencies of an RC coupled amplifier are 30Hz and 300Hz, respectively, find the gain relative to the mid-frequency gain at 60Hz and 600Hz. $(1+4+1+1)+2$